

# Circuits

- Kirchoff's rules
- Basic circuit elements
  - R, L, C
  - Units and time scales
  - Addition Rules
- Differential equation framework
- Common Circuit Types
- AC Circuits
  - Inductance
  - RLC circuit equation and solutions
- Other topics
  - Logic Gates

# Kirchoff's Laws

- Conservation of Charge  $\Leftrightarrow$  No net current flux at any point

$$\sum_i \vec{I}_i = 0$$

- Conservation of Energy  $\Leftrightarrow$  No net voltage over any loop

$$\sum_{Loop} V_i = 0$$

- Ohm's law

- Most general:  $\vec{J} = \sigma \vec{E}$

- More useful for circuits:

$$V = IR$$

$$V = IZ$$

# Basic Circuit Elements

- Remember how they affect voltages

$$V_R = IR$$

$$V_C = \frac{Q}{C} = \frac{1}{C} \int_0^t I(t') dt$$

$$V_L = L \frac{dI}{dt}$$

# Basic Circuit Elements

- Voltage drops  $\Leftrightarrow$  units

- $[R] = [V/I] = \text{JS}/\text{C}^2$

- $[C] = \text{C}/[V] = \text{C}^2/\text{J}$

- $[L] = [V/(I/S)] = \text{JS}^2/\text{C}^2$

$$V_R = IR$$

$$V_C = \frac{Q}{C} = \frac{1}{C} \int_0^t I(t') dt$$

- Time scales

- $[RC] = \text{S}$

- $[L/R] = \text{S}$

- $[LC] = \text{S}^2$

$$V_L = L \frac{dI}{dt}$$

- (Will be useful for circuits with time constants)

# Addition Rules

- R: Add in series

$$R_{total} = \sum_i R_i$$


- C: Add in parallel

$$\frac{1}{C_{total}} = \sum_i \frac{1}{C_i}$$

- L: Add in series

$$L_{total} = \sum_i L_i$$


# Example

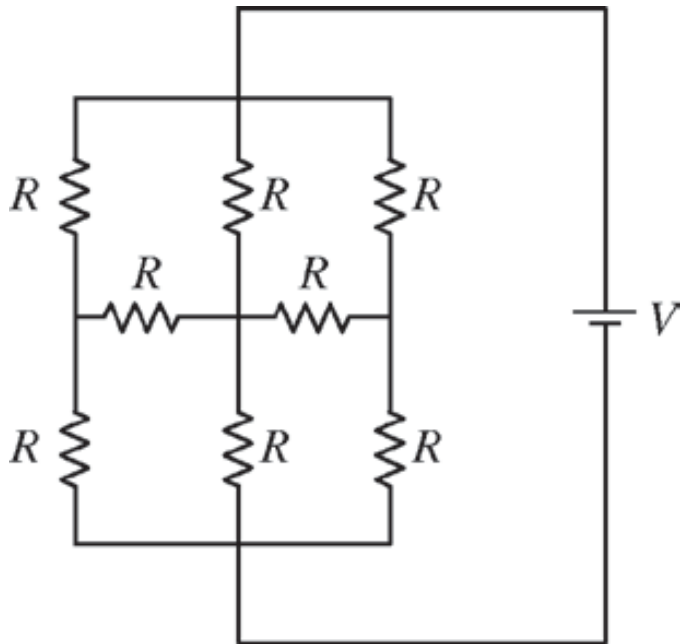

68. The circuit shown in the figure above consists of eight resistors, each with resistance  $R$ , and a battery with terminal voltage  $V$  and negligible internal resistance. What is the current flowing through the battery?

- (A)  $\frac{1}{3} \frac{V}{R}$
- (B)  $\frac{1}{2} \frac{V}{R}$
- (C)  $\frac{V}{R}$
- (D)  $\frac{3}{2} \frac{V}{R}$
- (E)  $3 \frac{V}{R}$


# Example

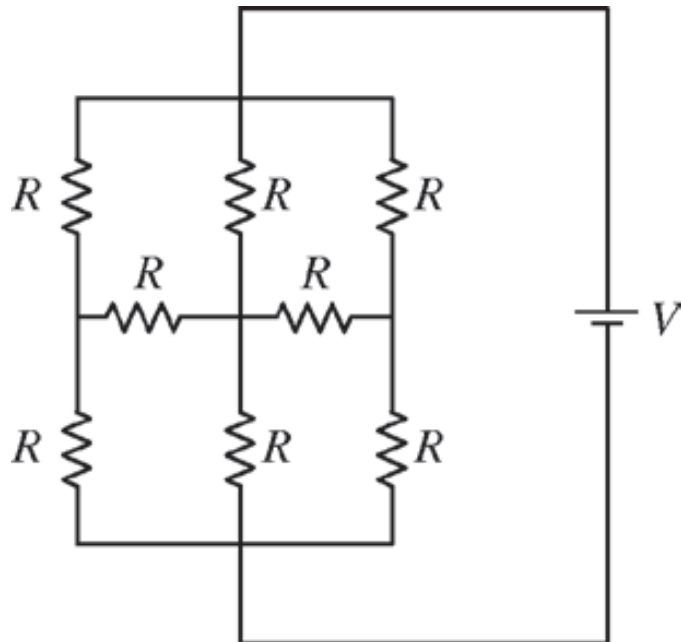

- What is the voltage drop across *each* of the resistors in parallel?
- What does this tell us about the voltage drop across the two center resistors
- (Related problem: symmetric resistor cube)
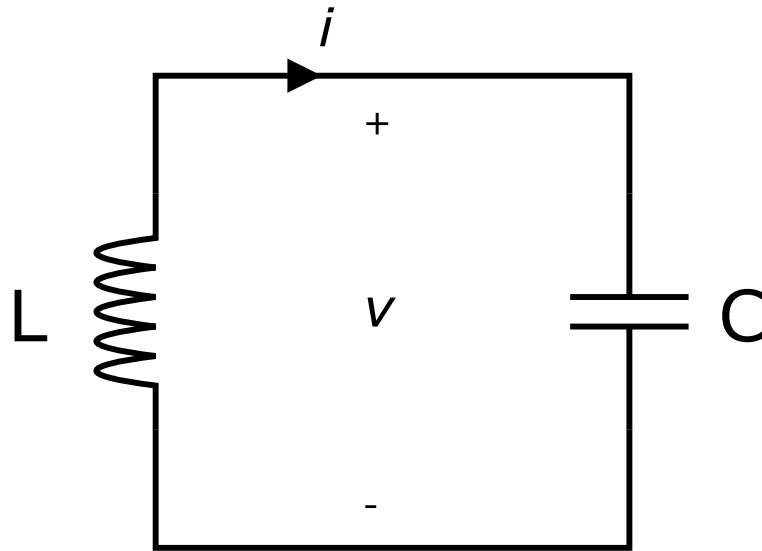
# Differential Equation Framework

- For a single loop in a circuit, we can use Kirchhoff's loop rule to write an ODE relating voltage drops across each element
- Example: LC Series Circuit





# Differential Equation Framework

- Voltage drop across capacitor vs time:


$$V_C = Q(t)/C$$

- Voltage drop across inductor vs time:

$$V_L = L \frac{dI}{dt} = L \frac{d^2 Q}{dt^2}$$

- Combine using loop rule:
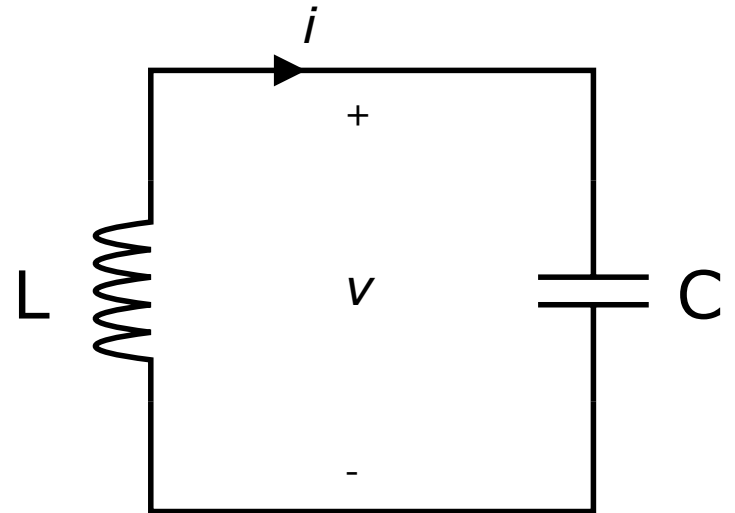
$$L \frac{d^2 Q}{dt^2} + \frac{1}{C} Q = 0$$




# LC Circuit ODE Example

59. For an inductor and capacitor connected in series, the equation describing the motion of charge is

$$L \frac{d^2 Q}{dt^2} + \frac{1}{C} Q = 0,$$

where  $L$  is the inductance,  $C$  is the capacitance, and  $Q$  is the charge. An analogous equation can be written for a simple harmonic oscillator with position  $x$ , mass  $m$ , and spring constant  $k$ . Which of the following correctly lists the mechanical analogs of  $L$ ,  $C$ , and  $Q$  ?

- |     | $\underline{L}$ | $\underline{C}$ | $\underline{Q}$ |
|-----|-----------------|-----------------|-----------------|
| (A) | $m$             | $k$             | $x$             |
| (B) | $m$             | $1/k$           | $x$             |
| (C) | $k$             | $x$             | $m$             |
| (D) | $1/k$           | $1/m$           | $x$             |
| (E) | $x$             | $1/k$           | $1/m$           |

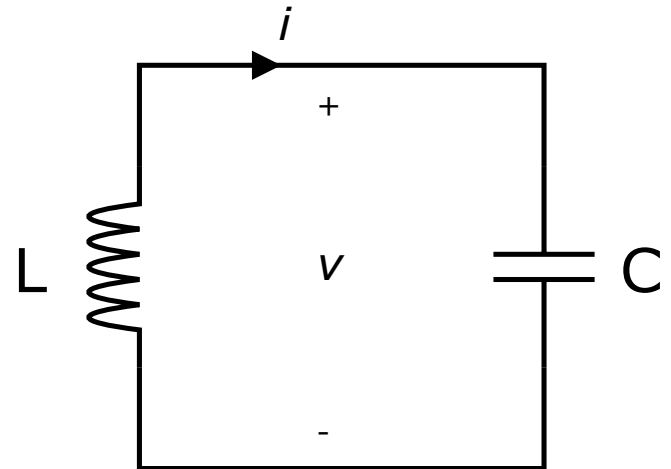

# LR Circuit Example


- (Ignore numerical values for  $R$ ,  $L$  for now)
- What is the voltage drop across  $R$ ?

$$V_R = RI(t)$$






- What is the voltage drop across  $L$ ?

$$V_L = L \frac{d^2 I}{dt^2}$$

$$V = RI + L \frac{dI}{dt}$$

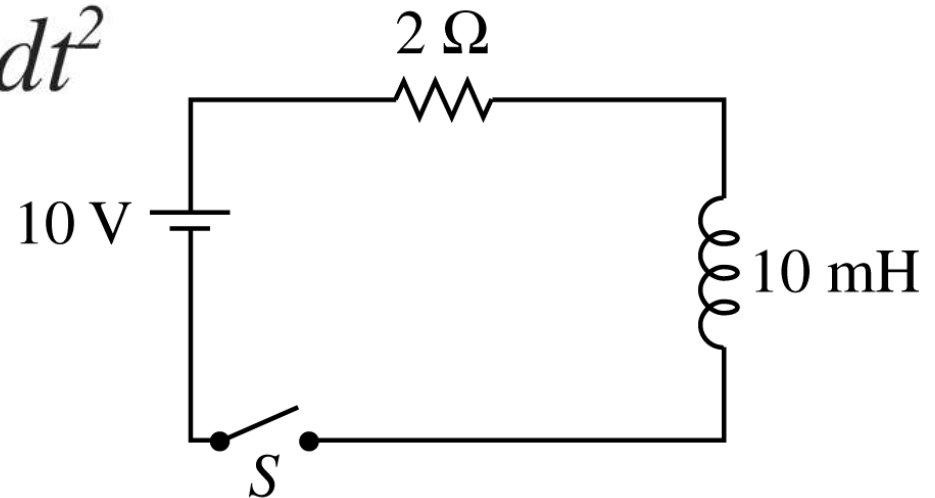


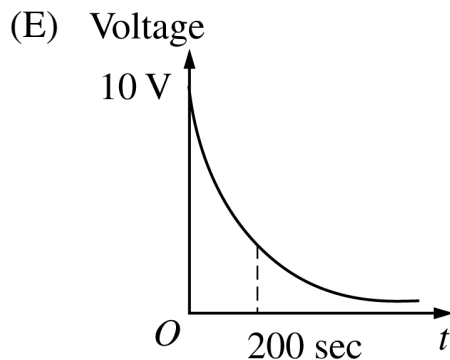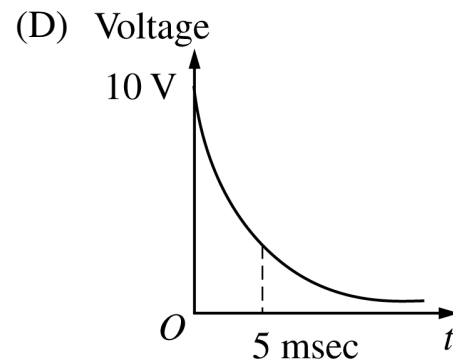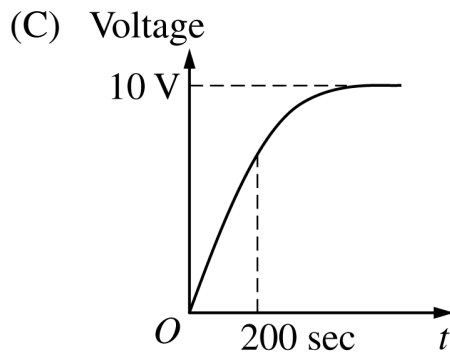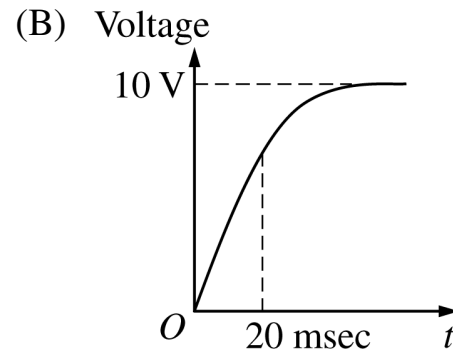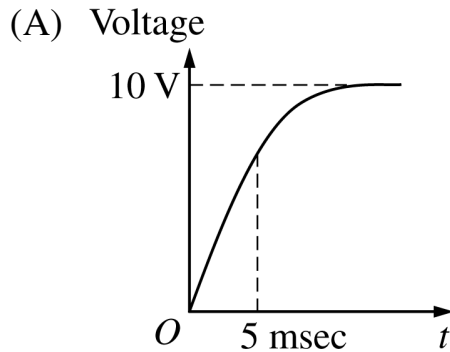40. In the circuit shown above, the switch  $S$  is closed at  $t = 0$ . Which of the following best represents the voltage across the inductor, as seen on an oscilloscope?



Time scale of solution?

$$V = RI + L \frac{dI}{dt}$$

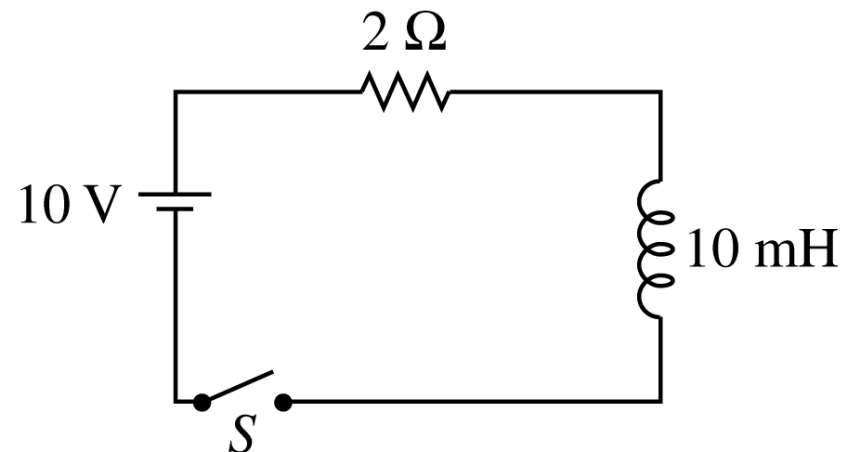

# RLC Circuits

$$\frac{Q}{C} + R \frac{dQ}{dt} + L \frac{d^2 Q}{dt^2} = 0$$

- Most general solution gives us damped oscillations

$$Q = Q_0 e^{-Rt/2L} \cos \left( \left( \sqrt{\frac{1}{LC} + \left( \frac{R}{2L} \right)^2} \right) t - \phi \right)$$

- Important to pay attention to boundary conditions
- Can remove terms based on other circuits

$$L=0 \quad \Rightarrow \quad \frac{Q}{C} + R \frac{dQ}{dt} = 0 \qquad C=0 \quad \Rightarrow \quad R \frac{dQ}{dt} + L \frac{d^2 Q}{dt^2} = RI + L \frac{dI}{dt} = 0$$

# Impedance

- Like resistance, but with a phase factor


$$V=IX_{RLC}$$

$$X_{RLC} = \sqrt{(X_L - X_C)^2 + R^2} = \sqrt{\left(\omega L - \frac{1}{\omega C}\right)^2 + R^2}$$


- Affects signal amplitude
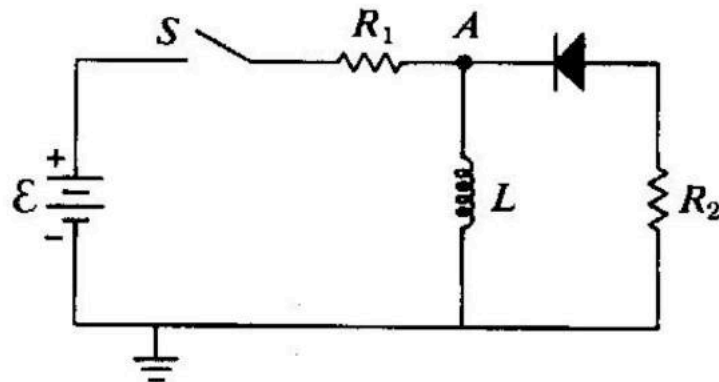
# Another Example

- What kind of behavior do circuit elements allow?



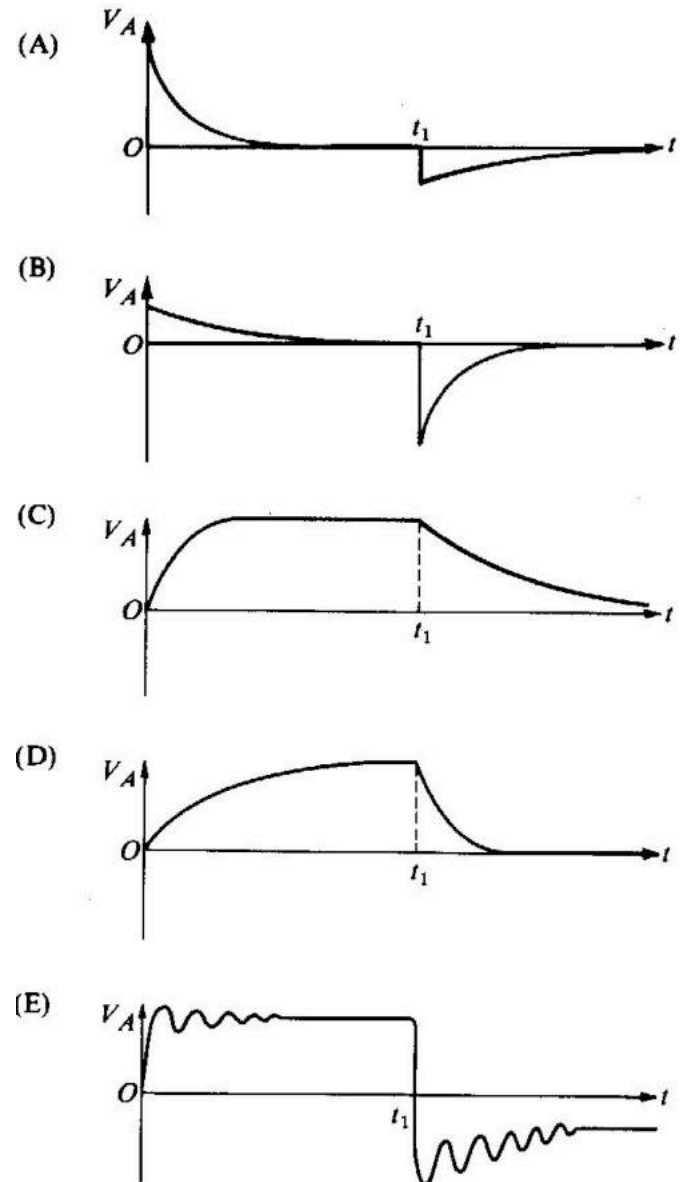94. In the circuit shown above,  $R_2 = 3R_1$  and the battery of emf  $\mathcal{E}$  has negligible internal resistance. The resistance of the diode when it allows current to pass through it is also negligible. At time  $t = 0$ , the switch  $S$  is closed and the currents and voltages are allowed to reach their asymptotic values. Then at time  $t_1$ , the switch is opened. Which of the following curves most nearly represents the potential at point  $A$  as a function of time  $t$ ?



# Another Example

- What is the starting charge on the capacitor?

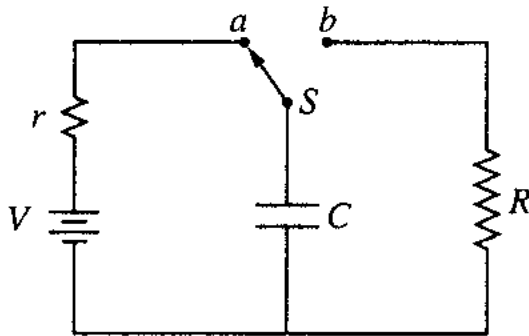


Figure 1

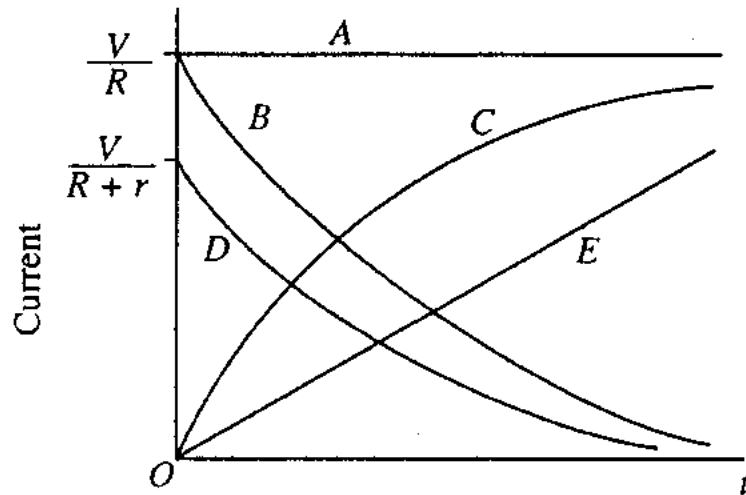


Figure 2

- The capacitor shown in Figure 1 above is charged by connecting switch  $S$  to contact  $a$ . If switch  $S$  is thrown to contact  $b$  at time  $t = 0$ , which of the curves in Figure 2 above represents the magnitude of the current through the resistor  $R$  as a function of time?

- (A) A
- (B) B
- (C) C
- (D) D
- (E) E